

# Companion Models for Basic Non-Linear and Transient Devices

Steven Herbst

July 8, 2008

## 1 PN Diode

As a two-terminal device with only one distinct operating region, the PN diode was a natural starting point for non-linear simulation. The current model does not include parasitic capacitances, but this is planned for the future.

The i-v relation that describes a diode is the following:

$$i(v) = I_S(e^{v/V_t} - 1) \quad (1)$$

where  $I_S$  is the reverse saturation current and  $V_t$  is the thermal voltage ( $kT/q$ ). From this, we derive the small-signal conductance:

$$g = \frac{di}{dv} = (I_S/V_t)e^{v/V_t} \approx i(v)/V_t \quad (2)$$

The error committed in the equation is  $I_S/V_t$ , which for common diodes is around  $10^{-12}S$ , which is negligible for common applications and allow us to avoid computing the exp function twice. In simulation we use the Newton-Raphson method to solve circuits with non-linear elements. The method works by linearizing the constitutive equations, solve for a new operating point, and iterate until convergence. The linearised curve around operating point  $v_n$  is :

$$i_{lin}(v) = i(v_n) + (di/dv)(v_n)(v - v_n) \quad (3)$$

By rearranging this equation, we find the i-v relation  $i_{lin} = (i(v_n) - gv_n) + gv$ . Hence the appropriate companion model for a diode is a conductance  $g$  in parallel with a current source  $i(v_n) - gv_n$ , not simply  $i(v_n)$ , as one might suspect. The result is shown in Figure ??.

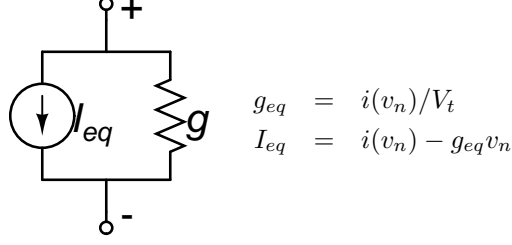


Figure 1: Linear companion model for diode

## 2 Metal-Oxide-Silicon Field-Effect Transistor

The next simplest non-linear devices are n- and p-channel MOSFETs, as no current flows into the gate, and the non-linear source-to-drain port depends on only two parameters,  $v_{GS}$  and  $v_{DS}$ . The model is complicated slightly, however, by the fact that MOSFETs have three distinct operating regions. For brevity, we derive only the results for n-channel MOSFETs. Similar results for p-channel MOSFETs are presented at the end of this section.

### 2.1 Cutoff: $v_{GS} - V_T < 0$

Cutoff is a trivial operating region, as all of the companion model parameters (depicted in Fig. ??) zero. No current flows into any of the nodes.

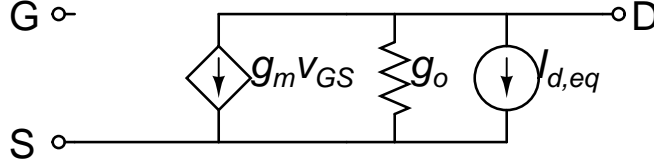


Figure 2: Linear companion model for n-channel MOSFET

### 2.2 Saturation: $0 \leq v_{GS} - V_T < v_{DS}$

In saturation, the following large-signal model holds:

$$I_D = \frac{K}{2}(v_{GS} - V_T)^2(1 + (v_{DS} - v_{DS,sat})/V_a) \quad (4)$$

where  $V_a$  is the Early voltage and  $v_{DS,sat} = v_{GS} - V_T$ . Since  $I_D$  is a function of two variables, we now use partial derivatives to find the small-signal conductances across the DS port.

$$g_m = \frac{\partial I_D}{\partial v_{GS}} = K(v_{GS} - V_T)(1 + (v_{DS} - v_{DS,sat})/V_a) = \sqrt{2KI_D} \quad (5)$$

$$g_o = \frac{\partial I_D}{\partial v_{DS}} = \frac{K}{2}(v_{GS} - V_T)^2/V_a = I_S/V_a \quad (6)$$

We seek to define a bias current from drain to source that will cause the node voltages to evolve by Newton-Raphson iteration, as we did for the diode in the previous section. We now use the multivariable form of the iteration equation:

$$I_{D,n+1} = I_D + g_m(v_{GS,n+1} - v_{GS,n}) + g_o(v_{DS,n+1} - v_{DS,n}) \quad (7)$$

Rearranging this equation, we find that  $I_{D,n+1} = (I_D - g_mv_{GS,n} - g_ov_{DS,n}) + g_mv_{GS,n+1} + g_ov_{DS,n+1}$ . Hence the bias current is  $I_{D,eq} = I_D - g_mv_{GS,n} - g_ov_{DS,n}$ . Although we will not derive it here, it should now be apparent that the following general result holds when determining bias currents for Newton-Raphson iteration:

$$I_{eq} = I(\mathcal{V}_i) - \sum_{v \in \mathcal{V}} \frac{\partial I}{\partial v} v_i \quad (8)$$

where  $\mathcal{V}$  is the set of device port voltages and  $\mathcal{V}_i$  is the set of calculated node voltages from the previous iteration.

### 2.3 Triode: $0 \leq v_{DS} \leq v_{GS} - V_T$

The drain current in this operating region is related to the  $v_{GS}$  and  $v_{DS}$  by Equation ???. Note that this model does not include the Early effect.

$$I_S = K((v_{GS} - V_T) - v_{DS}/2)v_{DS} \quad (9)$$

Applying partial derivatives, we find the small-signal conductances:

$$g_m = \frac{\partial I_D}{\partial v_{GS}} = Kv_{DS} \quad (10)$$

$$g_o = \frac{\partial I_D}{\partial v_{DS}} = K((v_{GS} - V_T) - v_{DS}) \quad (11)$$

Again,  $I_{D,eq} = I_D - g_mv_{GS} - g_ov_{DS}$ .

## 2.4 p-channel Results

The linear companion model for a p-channel MOSFET is shown in Figure ??, and the values of  $g_m$ ,  $g_o$ , and  $I_{S,eq}$  for the various operating regions are summarized in Table ?. For all operating regions,  $I_{S,eq}$  is related to  $I_S$ ,  $g_m$ , and  $g_o$  by the following equation:

$$I_{S,eq} = I_S - g_m v_{SG} - g_o v_{SD} \quad (12)$$

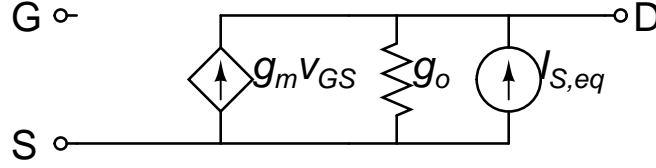


Figure 3: Linear companion model for p-channel MOSFET

Table 1: PMOS companion model parameters

Operating Region	Parameters
Cutoff: $v_{SG} - V_T < 0$	$I_S = 0$ $g_m = 0$ $g_o = 0$
Saturation: $0 \leq v_{GS} - V_T < v_{DS}$	$I_S = \frac{K}{2}(v_{SG} - V_T)^2(1 + (v_{SD} - v_{SD,sat})/V_a)$ $g_m = \sqrt{2KI_S}$ $g_o = I_S/V_a$
Triode: $0 \leq v_{DS} \leq v_{GS} - V_T$	$I_S = K((v_{SG} - V_T) - v_{SD}/2)v_{SD}$ $g_m = Kv_{SD}$ $g_o = K((v_{SG} - V_T) - v_{SD})$

### 3 Bipolar Junction Transistor

Companion models for BJTs are the most complex circuits presented here because current flows between all nodes. The model is not quite as unwieldy as it looks, however, because there is only one operating region.

We start with a simplified, mid-band Gummel-Poon NPN model, as shown in Figure ???. The base currents are defined as follows:

$$i_{bf} = (I_{fs}/\beta_f)(e^{v_{BE}/V_t} - 1) \quad (13)$$

$$i_{br} = (I_{rs}/\beta_r)(e^{v_{BC}/V_t} - 1) \quad (14)$$

Then, defining the small-signal conductances as in Figure ??, we have

$$g_{\pi,f} = \frac{\partial i_{bf}}{\partial v_{BE}} = (I_{fs}/\beta_f)e^{v_{BE}/V_t}/V_t \approx I_{bf}/V_t \quad (15)$$

$$g_{\pi,r} = \frac{\partial i_{br}}{\partial v_{BC}} = (I_{rs}/\beta_r)e^{v_{BC}/V_t}/V_t \approx I_{br}/V_t \quad (16)$$

$$g_{m,f} = \frac{\partial i_C}{\partial v_{BE}} = I_{fs}e^{v_{BE}/V_t}/V_t = \beta_f g_{\pi,f} \quad (17)$$